

- C1. When a $25.0\text{-}\Omega$ resistor is connected across the terminals of a real battery, the current in the circuit is 0.477 A . If this resistor is then replaced by a $100\text{-}\Omega$ resistor, the current in the circuit changes to 0.120 A . Calculate the internal resistance and the emf of the battery.

resistance	emf
$0.210\ \Omega$	12.0V

$$\text{E} - I_1(r + R_1) = 0 \quad \text{from } \textcircled{1}$$

$$\text{E} = I_1(r + R_1) \quad \text{where } R_1 = 25.0\Omega$$

$$I_1 = 0.477\text{A}$$

$$\text{E} - I_2(r + R_2) = 0 \quad \text{from } \textcircled{2}$$

$$\text{E} = I_2(r + R_2) \quad \text{where } R_2 = 100\Omega$$

$$I_2 = 0.120\text{A}$$

so $I_1(r + R_1) = I_2(r + R_2)$ → from $\textcircled{1}$

$$I_1r + I_1R_1 = I_2r + I_2R_2$$

$$I_1r - I_2r = I_2R_2 - I_1R_1$$

$$r = \frac{I_2R_2 - I_1R_1}{I_1 - I_2}$$

$$\text{E} = 0.477\text{A}(0.210\Omega + 25.0\Omega)$$

$$\text{E} = 12.0\text{V}$$

$$r = \frac{(0.120\text{A})(100\Omega) - (0.477\text{A})(25.0\Omega)}{0.477\text{A} - 0.120\text{A}}$$

$$r = 0.210\ \Omega$$